Raspberry Pi Internet of Things - part 14

Rolling my own I²C and 1-Wire interface card




VINNIE MOSCARITOLO JUN 21, 2025







Share

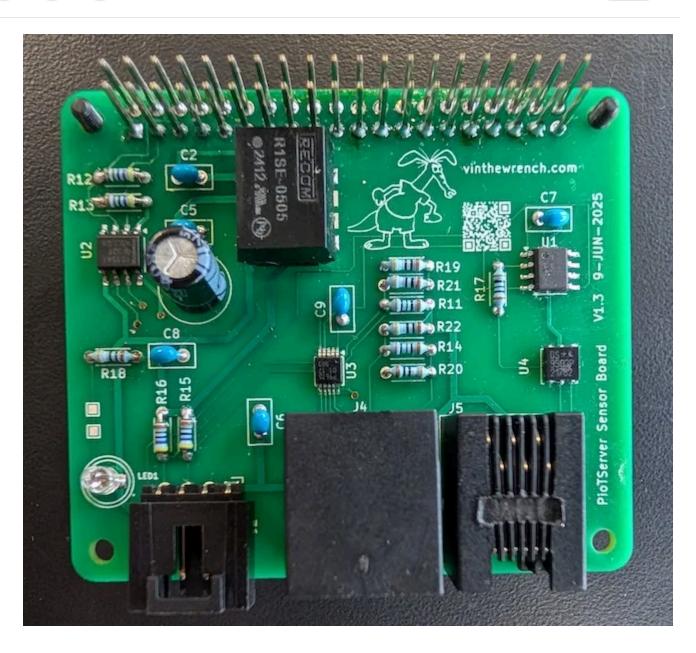

Earlier in this series, I wrote about how I used the I²C and Dallas 1-Wire protocol to communicate with the various sensors attached to my Raspberry Pi. In the process building and deploying my prototype, I became concerned with protecting the Raspberry Pi board from electrostatic discharge (ESD). I experimented with various interface cards from NCD, SparkFun, and AB Electronics.

I especially appreciated how \underline{NCD} utilized a TI $\underline{ISO1541}$ to shield the SCL and SDA $\underline{I^2C}$ signals, as well as an isolated $\underline{DC/DC}$ power supply. This was one of the best wa to prevent spikes on the $\underline{I^2C}$ power from propagating back to the Pi.

Another problem on my list was that some of the I²C devices I needed to communic with were situated farther away than the specification's recommended distance. I wable to overcome this limitation in a <u>previous project</u> by utilizing a <u>mini module frc Sparkfun</u> that utilized the PCA9615 to convert I²C signals to differential signals. I a tried the <u>1-Wire Pi Plus</u> board from <u>AB Electronics in the UK</u> to protect the Pi fron electrostatic discharge (ESD).

All these devices worked as a proof of concept, but assembling them was somewhat a hack. I needed something better since I planned to reproduce this arrangement several times on the farm.


So I dug deep into the product data sheets and articles from <u>Texas Instruments</u>, <u>NX Semiconductors</u>, and <u>RECOM Power</u>. I spent some time analyzing the manufacture reference designs; you can learn a great deal about how they intended the chips to be used. Using them, I was able to design my own Raspberry Pi add-on board, which combined the I²C and 1-Wire functions with proper ESD isolation.

Power supply isolation

The first thing I wanted to do was to protect the power that feeds the Raspberry Pi from any spikes or even shorts that might occur on the I²C and 1-Wire cables. I selected the R1SE-05050 DC/DC converters from RECOM Power. The R1SE-05050

takes the Raspberry Pi's +5V and produces 5V with approximately 1 kV of isolation. This device costs approximately \$3.50 at Mouser (all prices are for a quantity of 25).

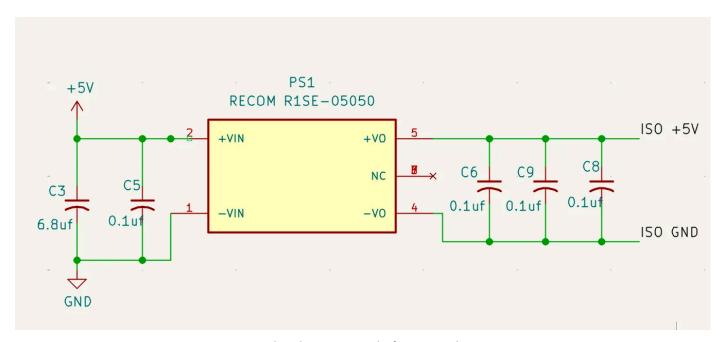I highly recommend that anyone involved in circuit design download <u>their books or power supply design and EMC</u>.



Isolated power supply for I2C and 1-Wire

I²C Isolation


I used the <u>ISO1541</u> to isolate and protect the Raspberry Pi's I²C SCL/SDA signals. <u>Texas Instruments provides a wealth of information</u> on protecting I²C on their website. The chip also allowed me to level-shift the SCL/SDA signals from 3.3V to a more robust 5V, and also make them compatible with NCD's <u>nodeLynk</u> devices.

One thing to keep in mind is that there are two versions of this product available ISO1540 and ISO1541. They are slightly different. The ISO1540 has two isolated bidirectional channels for SCL and SDA, while the ISO1541 has one bidirectiona data channel for SDA and a unidirectional clock channel for SCL. What this mea is that if you use the ISO1541, you must be careful to route the correct signals to chip when laying out your board. (*Ask me how I know!*)

The ISO1541DR costs about \$2.61 from Mouser, and the Molex socket compatible v NCD's nodeLynk costs about \$0.95

I²C Differential Driver

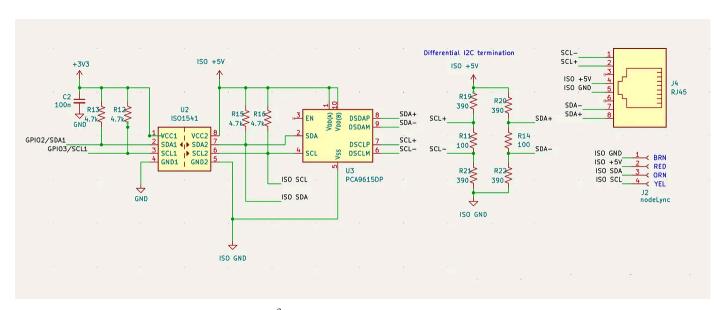I wanted to add the capability to communicate I²C over longer distances. (For detail please see the <u>section on extending I²C distance in part 4 of this series</u>.) For this, I the <u>NXP PCA9615DP</u> Differential I²C-Bus Buffer. The chip cost was approximately \$2.60, excluding the costs of a few resistors and an RJ45 connector.




I²C isolation and Differential driver

I powered the PCA9615 from the isolated 5V power supply. I also chose a 390/100/39 Ω bias resistor network so that it would be compatible with a <u>SparkFun QwiicBus</u> <u>EndPoint</u> on the receiving side. (For more information on the resistor choice, see the <u>PCA9615 datasheet section 7.2. on dI2C-bus side differential pair</u>)

If you plan to connect it to a SparkFun device, remember that QwiicBus devices operate at 3.3V, not 5V.

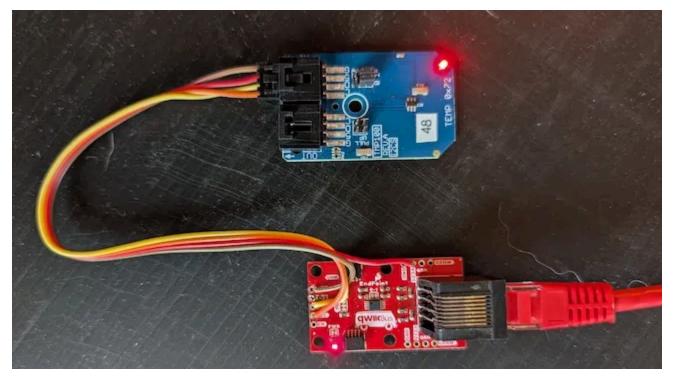Rather than using the QwiicBus connectors, I soldered a cable with 4-pin Molex SL 70553 2.54mm connectors that could be directly connected to a nodeLynk device.



Sparkfun Endpoint to nodeLynk

Note that the nodeLynk cables are configured to go from the OUT→ of one nodeLy device to the →IN of the next device. It took me a minute to realize that I could connect the cables backwards. You will know that you are doing it wrong if the LEI on the nodeLynk board is not lit brightly. The proper cable colors configuration is:


- RED 5V
- BRN GND
- ORN SDA
- YEL SCL

Also, if you look at the photo above, you will see that I hooked up the RED wire to t <u>VCC1 pin of the Endpoint</u>. I am still experimenting with this setup. I suspect that I could use some of the STEMMA 4 Pin JST SH devices directly at 5V.

1-Wire Interface

Since I use the <u>DS18B20</u> temperature sensors in my farm automation, I also need to protect the 1-Wire interface system. In my <u>article about 1-Wire</u>, I discussed why I selected the DS2482S-100+ 1-Wire Master over going directly to the Raspberry Pi GPIO line. Integrating this chip into my design was relatively easy; however, I also added the <u>DS9503P ESD Protection Diode</u>, which gave my circuit approximately 27 of isolation.

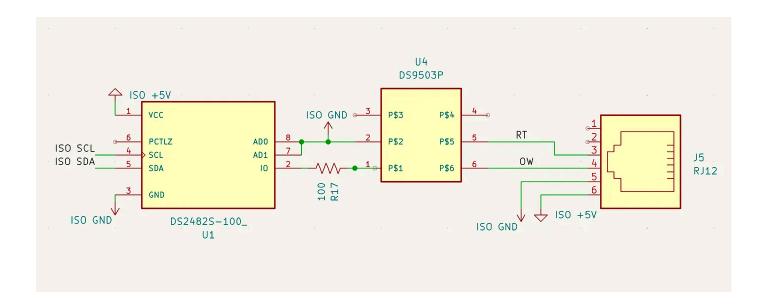The <u>DS2482S-100+ cost was about \$1.80</u>, and the <u>DS9503P around \$1.54</u>.



For this design, I used an RJ12 connector; however, anything with 3 or 4 pins would suffice. If you use an RJ12, the 6P6C color code is as follows:

- GRN ISO +5V
- ORN ISO GND
- BLU/WHT OW
- BLU -RT

PCB and Schematic Design


I have an on-and-off romance with designing circuits and PC boards, and have used variety of different CAD systems over the last 50 years. How do I say it, they all sucl

some more than others. I suppose the current rage is <u>KiCad</u> (maybe pronounced "ke KAD"). "That's all I have to say about that."

I posted the schematic and KiCad-compatible sources for making your board on my GitHub site.

While several companies will take the Gerber files generated from KiCad and send back a bare printed circuit board, I wanted one that not only has a good reputation also operates in the USA, preferably as a small business. I found that Sunstone Circuits, based in Oregon, was running the online site <u>easypcbusa.com</u>.

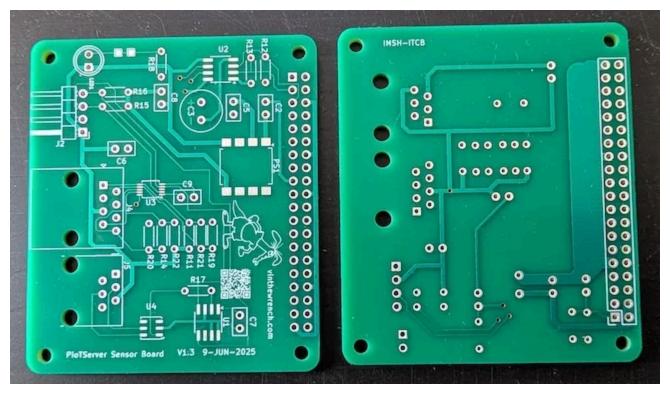EasyPCB was able to take the design file produced by KiCad and deliver a high-qua board for me for approximately \$10 per board with a 2-day build time. (Sadly, the U takes a week to get them from Oregon to Arkansas, but that's another saga of its ow




Bare boards from EasyPCB

Board Assembly

Populating the boards was not exceptionally difficult. I needed to brush up on my SMD soldering skills, but after a few minutes, I got the hang of it. Some of the SME parts, such as the RECOM DC/DC unit and the DS9503P, were a bit challenging du the pad layout. For these, I used a <u>cheap hot-air rework station</u> and solder paste, bu for most parts, I was able to use a trusty old-school Weller soldering station.

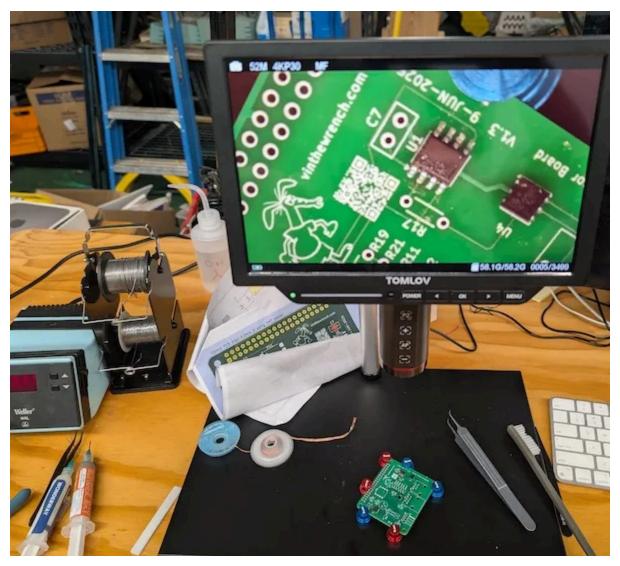Since I don't have the eyesight I had in my 20s, one thing I personally found very helpful was a digital microscope. I used to use a magnifying loupe to see any minuscule soldering remnants, but the microscope is so much easier to work with.



Digital microscopes rock!

There are lots of videos available online that demonstrate how to solder SMD parts One of my favorite videos is from David L. Jones from <u>EEVblog</u>.






Assembly and Design Verification

The design wasn't that complicated, but it took me two board revisions to get it correct. I tried to optimize my traces, and I thought I could get away with swapping the SCL/SDA signals going into the ISO1541. (see my note above about the SO1540 ISO1541). I was able to identify the problem quickly by tracing the signals using a locost digital oscilloscope. I had to cut and rework some of the traces, and once it was working, I updated my design and ran another small batch of boards from EasyPCE

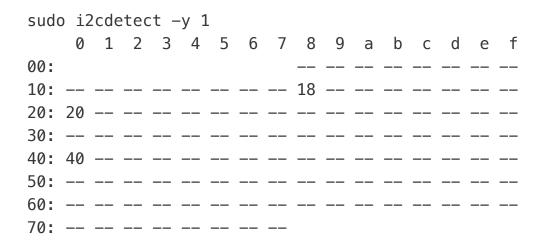Another helpful tool was the <u>i2cdetect</u> utility on the Raspberry Pi. The DS18B20 should appear as address 0x18. I also plugged in a few other I²C devices on known addresses, both on the isolated I²C and on the other end of the differential bus.



It will be fun, they said.

The final design of my own I²C interface card bill of materials came to a cost of approximately \$25 to \$30, excluding the cost of my engineering and assembly time. it was a valuable learning experience, and now that I have the skill mastered, I will likely design some additional boards in the future.

← Previous

Discussion about this post

Comments Restacks

Write a comment...

© 2025 Vinnie Moscaritolo • $\underline{\text{Privacy}}$ • $\underline{\text{Terms}}$ • $\underline{\text{Collection notice}}$ $\underline{\text{Substack}}$ is the home for great culture